

Differential Equations.

1st order diff. = 7/15 :-

①

1st order =

$$\frac{di}{dt} + a_1 i = C$$

nth order :-

$$a_0 \frac{d^n i}{dt^n} + a_1 \frac{d^{n-1} i}{dt^{n-1}} + \dots + a_{n-1} \frac{di}{dt} + a_n i = C$$


Homogeneous :-

1) $C = 0$ is given, d. eqn is homogeneous.

2) $C \neq 0$, d. eqn is non-homogeneous.

Linear :- A diff. = y is said to be linear if the dependent variable & all its derivatives are of first degree.

R-L CKT :-

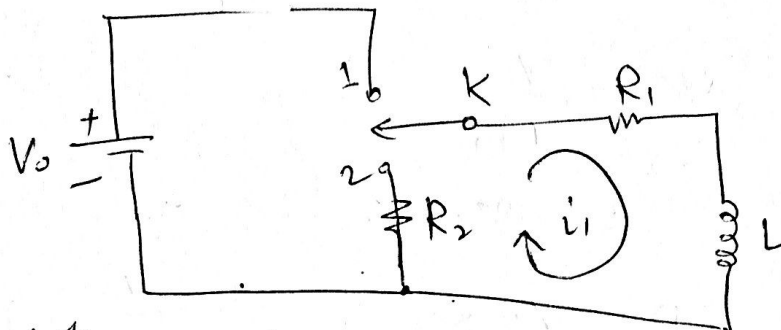

After $t=0$, switch is closed from P1 to P2

$$L \frac{di}{dt} + R i = 0$$

$$\text{or } \frac{di}{i} = \frac{-R}{L} dt$$

$$\text{on integration, } \ln i = -\frac{R}{L} t + \ln k$$

$$\ln i = \ln e^{-\frac{Rt}{L}} + \ln k$$

$$\ln i = \ln k \cdot e^{-\frac{Rt}{L}}$$

$$\Rightarrow \text{the gen } i = \text{gen } k \cdot e^{-\frac{Rt}{L}}$$

or ~~where~~
 $i = k \cdot e^{-t/\tau}$

$$\tau = L/R = \text{time constant}$$

→ i gen is general soln. since k is unknown.

→ To find k , initial conditions have to be taken into account & particular soln. is to be found.

Before switching at $t=0$,

$$i(0) = \frac{V_0}{R_1}$$

∴ at $t = \infty$,

$$\frac{V_0}{R_1} = \frac{V_0}{R_1} k \Rightarrow k = \left(\frac{V_0}{R_1} \right)$$

$$i = \frac{V_0}{R_1} e^{-\frac{Rt}{L}}$$

Soln. to a Non-homogeneous = γ using

Integrating factor :-

N-H = γ x

$$\frac{di}{dt} + Pi = Q$$

where P is a constant

& Q may be either $f(t)$ or const.

$$i = \underbrace{e^{-Pt} \int Q e^{Pt} dt}_{\text{particular integral}} + \underbrace{k e^{-Pt}}_{\text{complementary fn.}}$$

step voltage response of series R-L ckt :-

Let K be moved for 2 to 1 ct

$t = 0$; d.c. step of V_0 has been applied to R-L N/W.

Thus a d.c. step of V_0 has been applied to R-L N/W. \rightarrow on applying KVL to N/W, we get

$$L \frac{di}{dt} + Ri = V_0$$

$$\text{or } \frac{di}{dt} + \frac{R}{L} i = \frac{V_0}{L}$$

$$\text{Thus } P = \frac{R}{L} \quad \& \quad Q = \frac{V_0}{L}$$

$$i = e^{-Pt} \int \mathcal{Q} e^{Pt} dt + k e^{-Pt}$$

$$i = e^{-Rt/L} \int \frac{V_0}{L} e^{Rt/L} dt + k e^{-Rt/L}$$

$$= e^{-\frac{Rt}{L}} \cdot \frac{V_0}{L} \cdot e^{\frac{Rt}{L}} \cdot \frac{L}{R} + k e^{-Rt/L}$$

$$i = \frac{V_0}{R} + k e^{-\frac{Rt}{L}}$$

→ Applying initial condition that $i = 0$ before ~~the~~ & just after closing switching,


$$0 = \frac{V_0}{R} + k e^0$$

$$\Rightarrow k = -\frac{V_0}{R}$$

$$i = \frac{V_0}{R} - \frac{V_0}{R} e^{-Rt/L}$$

$$\Rightarrow i = \frac{V_0}{R} (1 - e^{-Rt/L})$$

$$= \frac{V_0}{R} (1 - e^{-t/\tau})$$

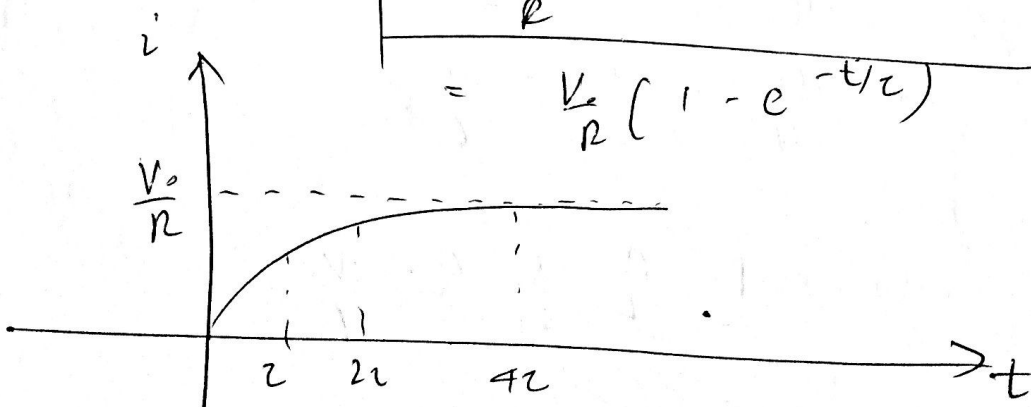

Time Constant :-

$$i = \frac{V_0}{R} e^{-t/\tau}$$

$$i = I_0 e^{-t/\tau}$$

$$\therefore \frac{i(t)}{I_0} = e^{-t/\tau}$$



At $t = \tau$,

$$\frac{i(t)}{I_0} = e^{-1} = 0.37 = 37\%$$

→ Thus ~~the~~ current reduces to 37% ↓ its initial value after a time interval equal to τ .


At $t = 4\tau$,

$$\frac{i(t)}{I_0} = e^{-4} = 0.02 = 2\%$$

Again,

if

$$i(t) = I_0 (1 - e^{-t/\tau})$$

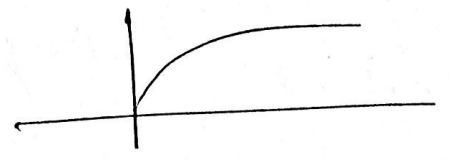

$$\Rightarrow \frac{i(t)}{I_0} = 1 - e^{-t/\tau}$$

At $t = \tau$


$$\frac{i(t)}{I_0} = 1 - e^{-1} = 1 - \frac{1}{e} = 0.63$$

= 63%

$\tau =$ in which I increases to 63%

Step voltage Response of series R-C circuit :-

Case I :-

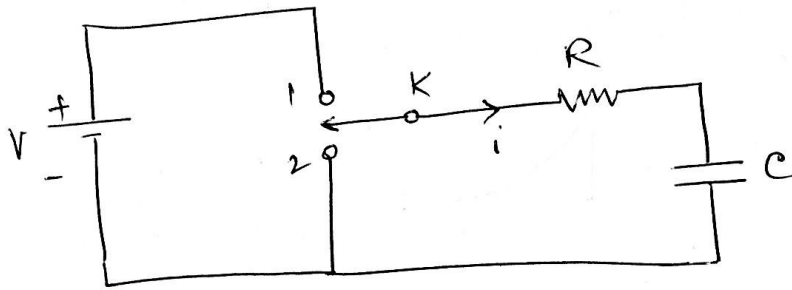

Case I :- K initially at position 1.
Then A. 2

After switching, KVL gives

$$\frac{1}{C} \int i dt + iR = 0$$

$$\Rightarrow R \frac{dq}{dt} + \frac{q}{C} = 0$$

$$\Rightarrow -\frac{1}{RC} dt = \frac{dq}{q}$$

Integrating B/s,

$$-\frac{1}{RC} \int dt = \int \frac{dq}{q}$$

$$\text{or } -\frac{t}{RC} = \ln q + \ln k$$

$$\Rightarrow q = k e^{-t/RC}$$

k is evaluated from initial condition
Before switching $q(0) = VC$


At $t=0$,

$$q = k = VC$$

$$\therefore q = K e^{-t/RC}$$

$$q_c = \frac{q}{C} = V \cdot e^{-t/RC}$$

$$q_c = V e^{-t/RC}$$

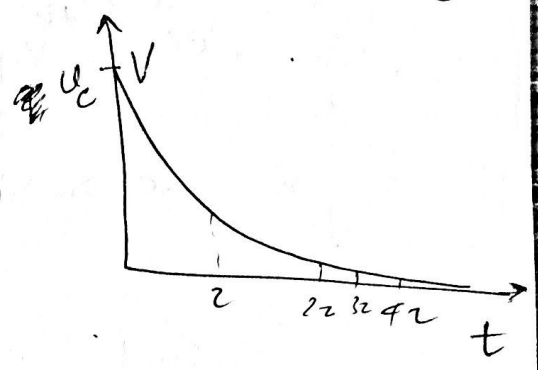

Case II \rightarrow Let initial position of switch be 2.
 Then switch to P1.
 Now entire voltage V gets applied to RC circuit.

Applying KV to this circuit,

$$iR + \frac{1}{C} \int i dt = V$$

$$\Rightarrow R \frac{di}{dt} + \frac{i}{C} = 0$$

$$\text{or } (-RC) \frac{di}{i} = dt$$

On integration -

$$-RC \ln i = t + K$$

conditions. \bullet K is known from initial conditions.
 At $t=0$ before switch \rightarrow after $q_c = 0$ hence after switch $i = V/R$
 $-RC \ln \frac{V}{R} = K$

$$\therefore -RC \ln \left(\frac{V}{R} \right) = k$$

$$\text{or } -RC \ln i = t - RC \ln \frac{V}{R}$$


$$\Rightarrow \ln \frac{i}{V/R} = \frac{-t}{RC}$$

$$\text{or } \frac{i}{V/R} = e^{-t/RC}$$

$$\text{or } i = \frac{V}{R} e^{-t/RC}$$

$$\text{or } i = I e^{-t/\tau}$$

$$\tau = RC$$

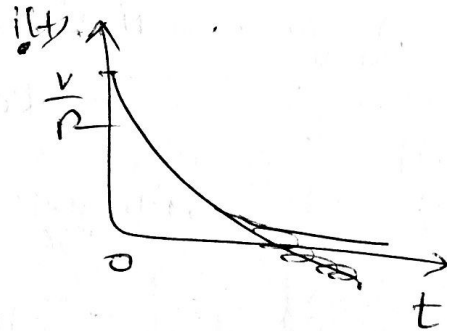

~~What is?~~

$$v_R = IR e^{-t/\tau}$$


$$= V e^{-t/\tau}$$

$$v_C = \frac{1}{C} \int i dt$$

$$\therefore v_C = V - V_R$$


$$= V - V e^{-t/\tau}$$

$$= V(1 - e^{-t/\tau})$$

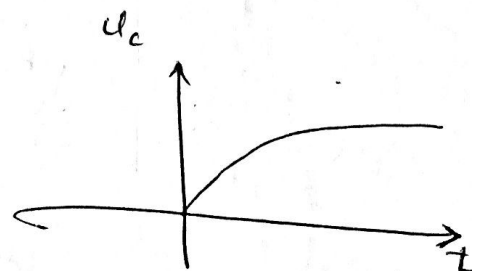

Assignment :- in class


(5)

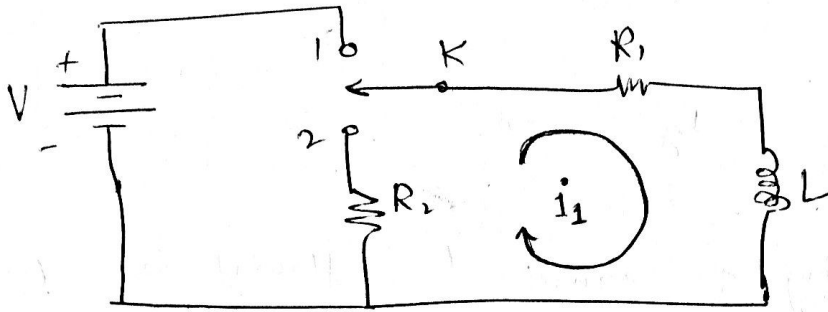

Find $i = ?$

$$i = \frac{V}{R_1} e^{-\frac{(R_1 + R_2)t}{L}}$$

Assignment for home :-

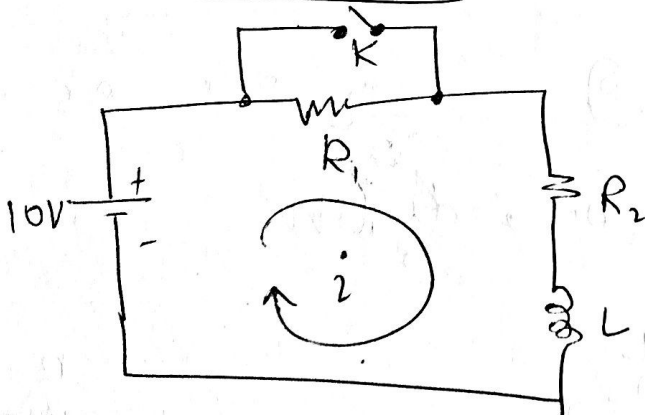

→ Switch K is closed at time $t=0$, steady state has reached. obtain expression for current in RL at any time t .

$$K = \frac{-VR_1}{R_1 + R_2}$$

$$i = \frac{V}{R_2} + K e^{-\frac{R_2 t}{L}}$$

$$i = \frac{V}{R_2} \left[1 - \frac{R_1}{R_1 + R_2} e^{-\frac{R_2 t}{L}} \right]$$

Initial Conditions :-

At $t = 0^+$,

(i) Replace every L by D.C.

or
a I. gen having I equal to flowing at $t = 0^+$.


(ii) Replace every C by S.C.

or
a V. gen having s.c. voltage V_0 equal to $\frac{q_0}{C}$
if there is an initial charge q_0 .

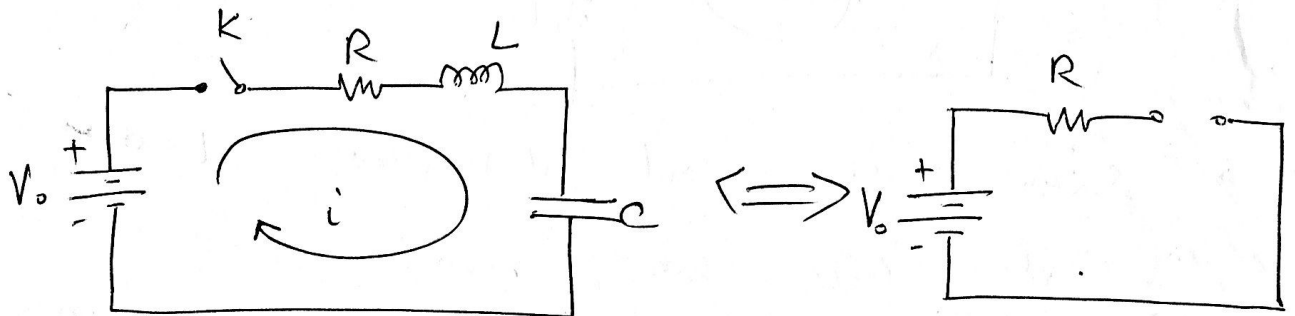(iii) Leave every R in the N/W unchanged.
from (6)

Initial conditions of a series RLC N/W :-

Assignment Find $i(0^+)$, $\frac{di}{dt}(0^+)$, $\frac{dq}{dt}(0^+)$



$i(0^+) = 0 \rightarrow$ by observation


$\frac{di(0^+)}{dt} = ?$ Applying KVL to N/W,

$$L \frac{di}{dt} + iR + \frac{1}{C} \int i dt = V_0$$

$$\Rightarrow L \frac{di}{dt} + iR + \frac{q}{C} = V_0 \quad \text{Put } q(0^+) = 0$$

$$\& \quad i(0^+) = 0 \quad \therefore L \frac{di(0^+)}{dt} + 0 + 0 = V_0 \quad \Rightarrow \frac{di(0^+)}{dt} = \frac{V_0}{L}$$

Assignment 1 :-

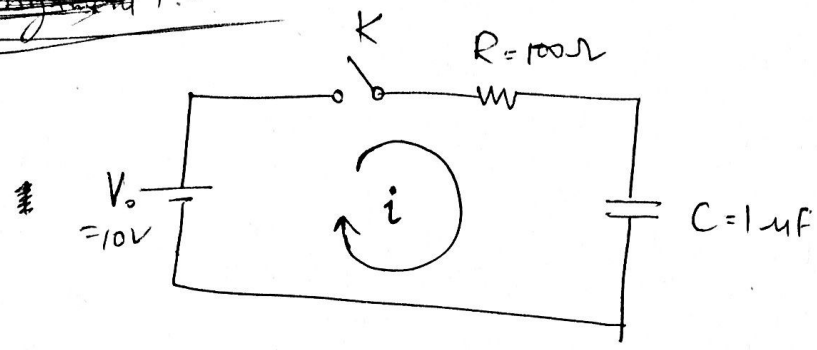

Find $i(0+)$ & $\frac{di}{dt}(0+)$.

$$V_0 = iR + \frac{q}{C}$$

$$0 = R \frac{dq}{dt} + \frac{1}{C}$$


$$\Rightarrow \frac{dq}{dt} = \frac{-1}{RC}$$

Soln :-


$$V_0 = iR + \frac{1}{C} \int i dt$$

$$i(0+) = \frac{V_0}{R} = \frac{10}{100} = 0.1 \text{ A}$$

$$\& \frac{di}{dt} = -\frac{1}{CR} \cdot i(0+) = \frac{-0.1}{(10^{-6} \times 100)}$$

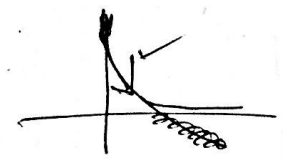

Assignment 2 :-

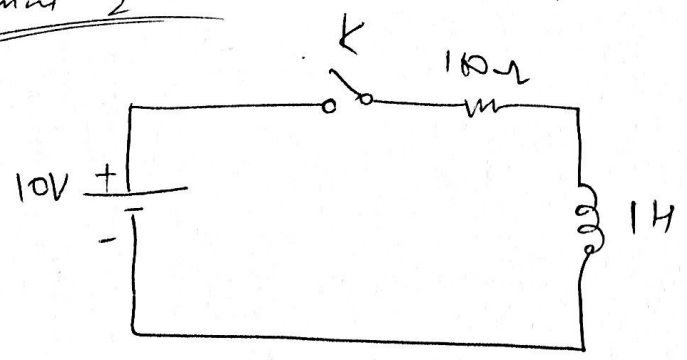

$$V_0 = iR + L \frac{di}{dt}$$


$$\Rightarrow i(0+) = 0$$

$$\frac{di}{dt}(0+) = \frac{V_0}{L}$$

$$= \frac{10}{1}$$

$$= 10 \text{ A/s}$$
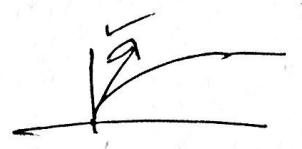
$$i(0+) = 0, \quad \frac{di}{dt}(0+) = 10 \text{ A/s}$$




~~$i(0+) = 0$~~

(7) ~~(8)~~


~~$L \frac{di(0+)}{dt} + 0 + 0 = V_0$~~

~~$\Rightarrow \frac{di(0+)}{dt} = \frac{V_0}{L}$~~

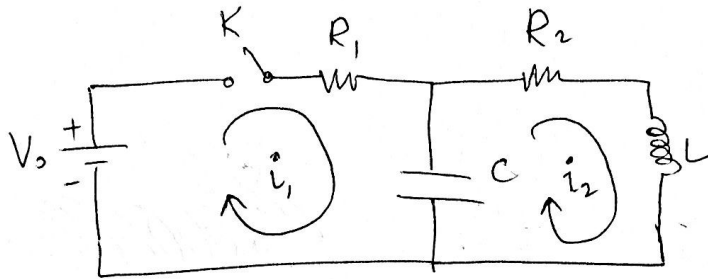Initial conditions in the case of a 2 mesh RLC circuit :-



At $t = (0+)$, circuit is :-

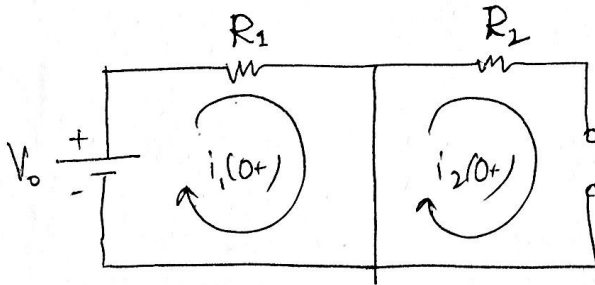

Find $i_1(0+)$, $i_2(0+)$, $\frac{di_1(0+)}{dt}$, $\frac{di_2(0+)}{dt}$.

\Rightarrow No initial voltage on C & no initial current thru L .

by inspection,

$i_2(0+) = 0$ & $i_1(0+) = \frac{V_0}{R_1}$

Applying KVL to NW

$$\frac{1}{c} \int (i_1 - i_2) dt + R_1 i_1 = V_0 \quad (1)$$

$$\& \underbrace{\frac{1}{c} \int (i_2 - i_1) dt}_{V \text{ rise for } c} - i_2 R_2 - L \frac{di_2}{dt} = 0$$

$$\text{or } \frac{1}{c} \int (i_1 - i_2) dt + i_2 R_2 + L \frac{di_2}{dt} = 0 \quad (2)$$

In (2), ^{zero} _{no} change & $i_2(0+) R_2 = 0$

$$\therefore \frac{di_2(0+)}{dt} = 0$$

In (1), we need $\frac{di_1(0+)}{dt}$

Differentiating (1), we have

$$\frac{(i_1 - i_2)}{c} + R_1 \frac{di_1}{dt} = 0$$

$$\text{At } t = 0+, \quad i_2(0+) = 0, \quad i_1(0+) = \frac{V_0}{R_1}$$

$$\therefore R_1 \frac{di_1(0+)}{dt} = -\frac{1}{c} \left[\frac{V_0}{R_1} \right]$$

$$\text{or } \boxed{\frac{di_1(0+)}{dt} = -\frac{V_0}{R_1^2 c}}$$

Now Assignment on \textcircled{S} Back