

Network Theorems & Impedance Functions:-

①

On Characteristic Eqn:

Consider a 2nd order homogeneous diff. eqn.
with constant coefficients :-

$$a_0 \frac{d^2 i}{dt^2} + a_1 \frac{di}{dt} + a_2 i = 0 \quad \rightarrow (1)$$

→ sum to this diff. eqn must be such that
the sum itself, its 1st derivative & its second
derivative, each multiplied by a constant
coeff. add-up to zero.

This is possible when all 3 terms must
be of the same form, differing only in
their coeff's.

→ gen. sol. always leads by rever to eqn,

$$i(t) = k e^{st} - s$$

where k & s are constants which may
be real, imag., or complex.

Subs. (2) in (1), we have

$$a_0 s^2 k e^{st} + a_1 s k e^{st} + a_2 k e^{st} = 0$$

$$\Rightarrow a_0 s^2 + a_1 s + a_2 = 0$$

This eqn is oft. an auxiliary eqn.

s is a bi-valued root of aux. eqn.

s is the complex freq.

B.Tech.ELE :-

Transform Impedance / admittance transform CKTS :-

xform impedance of ele. elements namely

R, L & C.

(a) Resistance :-

for an R,

$$U_R(t) = R \cdot i_R(t)$$

$$i_R(t) = G \cdot U_R(t)$$


Transform ~~by direct~~ is

$$V_R(s) = R \cdot I_R(s)$$


Xform impedance of an R is given by

$$\boxed{Z_R(s) = R = \frac{V_R(s)}{I_R(s)}} \Rightarrow Y_R(s) = G = \frac{1}{R}$$

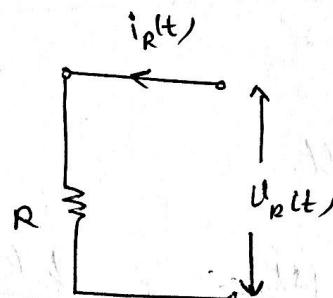→ Thus an R is insensitive to even the complex frequency.



(a) R in Time-Domain

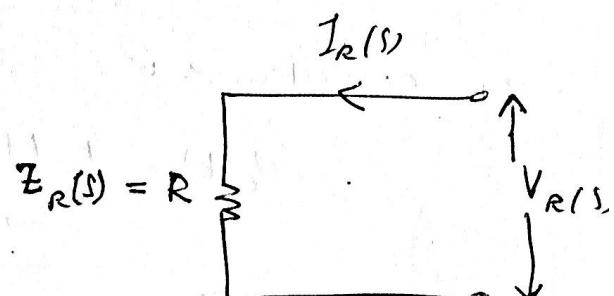

(b) Transform representation
of resistor

revision

(b) Inductance :- for an L ,

$$V_L(t) = L \cdot \frac{di_L(t)}{dt}$$

or $\frac{d}{dt}$


$$\text{or } V_L(s) = L [s I_L(s) - i_L(0+)]$$

if $i_L(0+) = 0$, then

$$Z_L(s) = \frac{V_L(s)}{I_L(s)} = Ls$$


IIIly,

$$Y_L = \frac{1}{Ls}$$

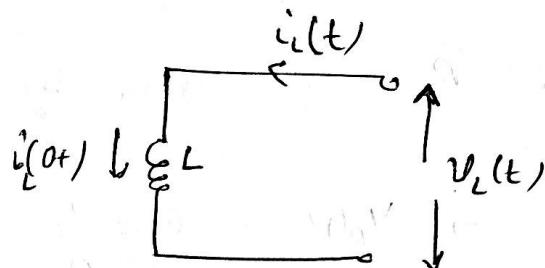

(a) L with initial current

$$i_L(0+)$$

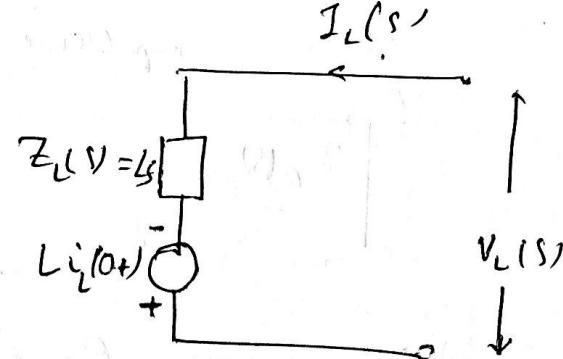

(b) from representation


(c) Capacitance :-


$$Q_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t) dt$$

$$\text{or } V_c(s) = \frac{1}{C} \left[\frac{I_c(s)}{s} + \frac{q(0+)}{s} \right]$$

where capacitor $q(0+)$ is initial charge across


$$\frac{q(0+)}{C} = Q_c(0+)$$

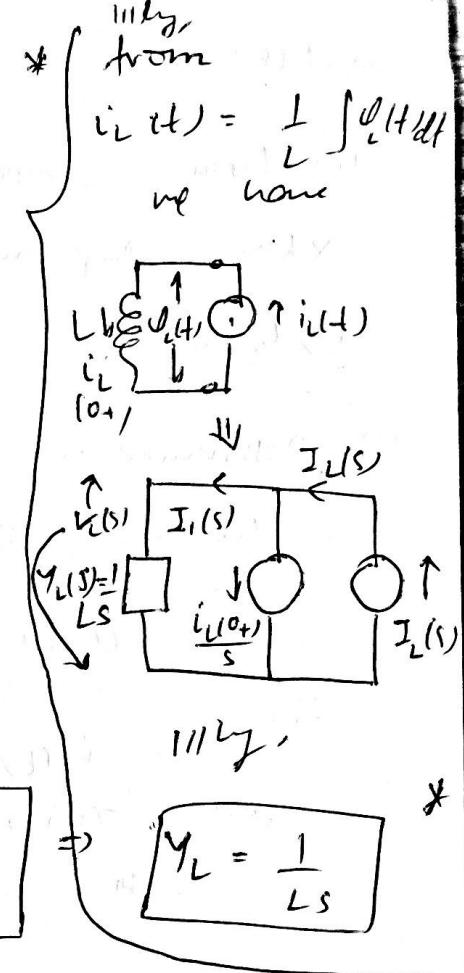

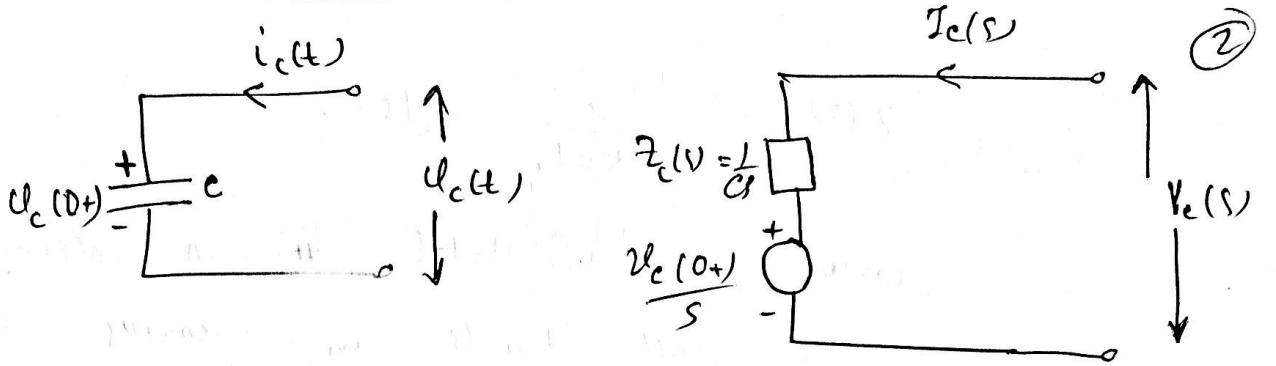


(a) T-D. representation

if $C \in$ initial voltage

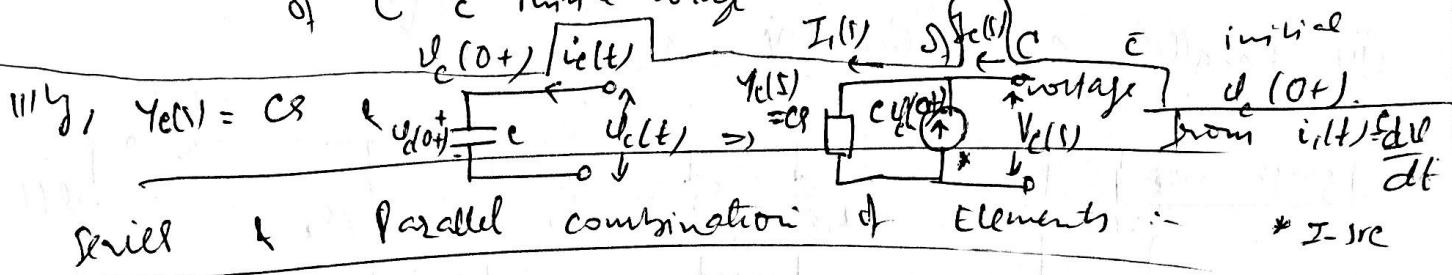

Series & Parallel combination of Elements :- * I-src

(i) Series combination :-

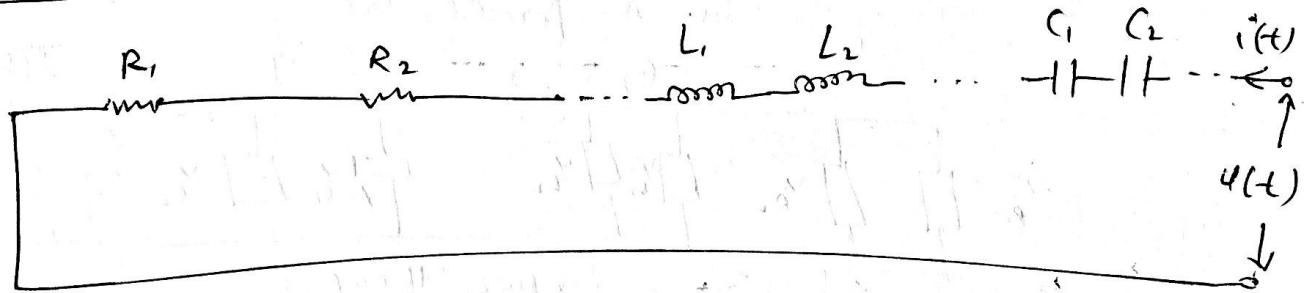

Now,

$$v(t) = v_{R_1} + v_{R_2} + \dots + v_{L_1} + v_{L_2} + \dots + v_{C_1} + v_{C_2} + \dots \quad (1)$$

L. Xfrm given

$$V(s) = V_{R_1}(s) + V_{R_2}(s) + \dots + V_{L_1}(s) + V_{L_2}(s) + \dots + V_{C_1}(s) + V_{C_2}(s) + \dots \quad (2)$$

using B/S S) (1), by $I(s)$, we have $\quad (2)$


$$\begin{aligned} Z(s) = & Z_{R_1}(s) + Z_{R_2}(s) + \dots + Z_{L_1}(s) + Z_{L_2}(s) + \dots \\ & + Z_{C_1}(s) + Z_{C_2}(s) + \dots \end{aligned} \quad (3)$$

$$\text{or } Z(s) = \sum_{k=1}^n Z_k(s)$$


where n is total # of elements*

of all kinds in series

(ii) Parallel Combination of elements :-

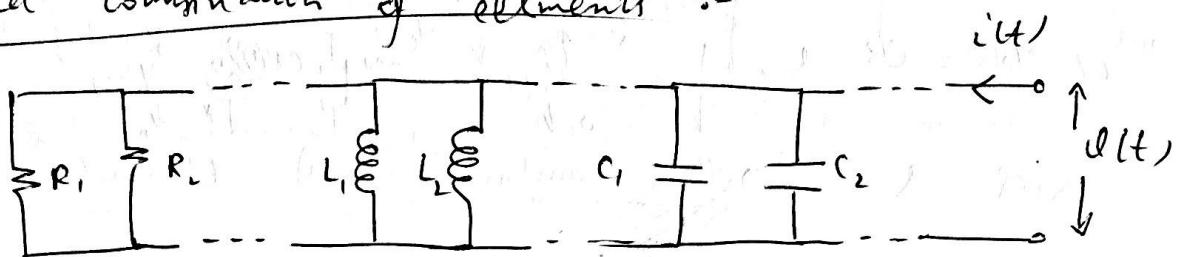

(a) A parallel cut

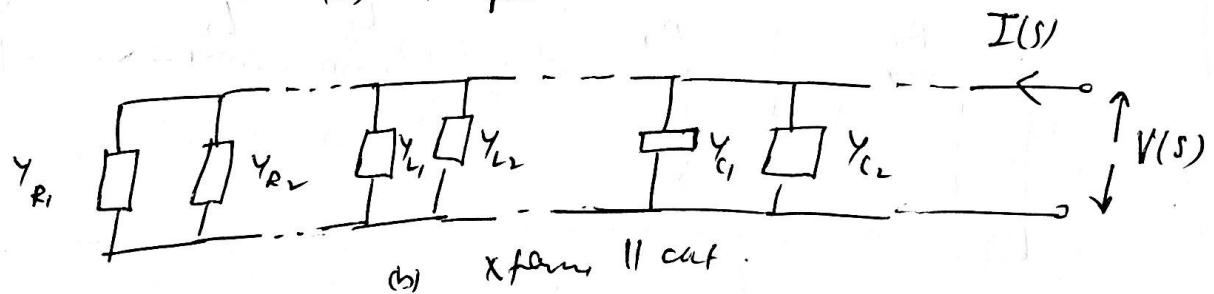

(b) X-form II cut.

Here from cut (a),

$$i(t) = i_{R_1}(t) + i_{R_2}(t) + \dots + i_{L_1}(t) + i_{L_2}(t) + \dots + i_{C_1}(t) + i_{C_2}(t),$$

Taking Δ -X form of (b), we have — (1)

$$I(s) = I_{R_1}(s) + I_{R_2}(s) + \dots + I_{L_1}(s) + I_{L_2}(s) + \dots + I_{C_1}(s) + I_{C_2}(s) + \dots$$


Dividing B/S of (2) by $V(s)$, we get — (2)

$$Y(s) = Y_{R_1}(s) + Y_{R_2}(s) + \dots + Y_{L_1}(s) + Y_{L_2}(s) + \dots + Y_{C_1}(s) + Y_{C_2}(s) + \dots$$

$$\text{or } Y(s) = \sum_{k=1}^n Y_k(s)$$

where n is # of elements in parallel

(3)

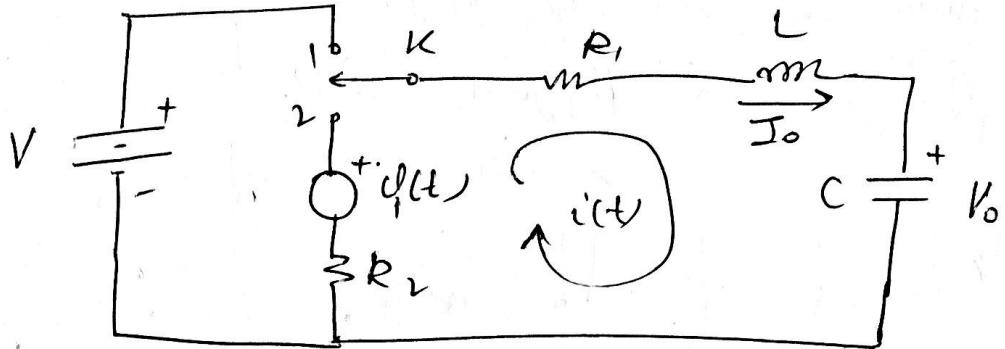Example


K is moved from P_1 to P_2 at $t = 0$.

$$\text{At } t = 0^-, \quad i_0(0^-) = I_0$$

$$\text{& } v_0(0^-) = V_0$$

At $t = 0^+$, voltage src $v_0(t)$ & resistor R_2 get connected to the $R-L-C$ circuit.

Find $I(s)$ & $i(t)$

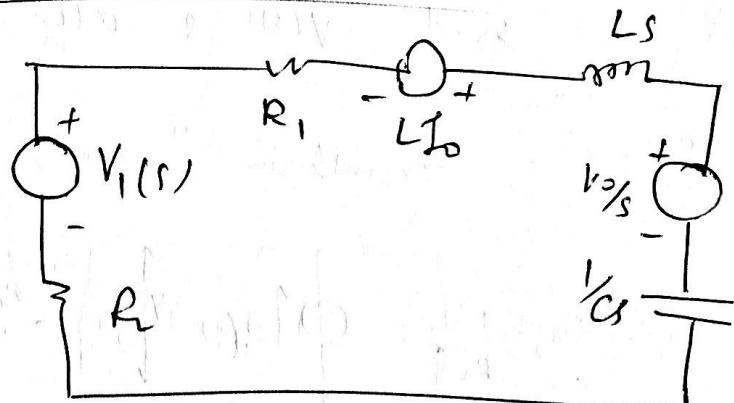Soln :-~~W.L.G.~~

Eg. xform cat.

Total transform voltage in N/W is given by

$$V(s) = V_1(s) + L I_0 - \frac{V_0}{s}$$

Total xfrm current is


$$Z(s) = R_1 + R_2 + Ls + \frac{1}{sC}$$

Xfrm current is given by

$$I(V) = \frac{V(s)}{Z(s)} = \frac{V_1(s) + L I_0 - \frac{V_0}{s}}{R_1 + R_2 + Ls + \frac{1}{sC}}$$

This can be expanded using P.F. method
if on \mathcal{L}^{-1} it gives $i(t)$.

(#)

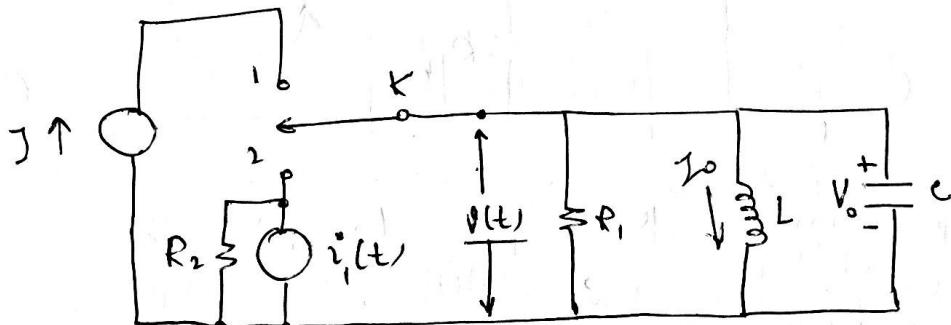


K is moved from π_1 to π_2 at $t=0$.

$$i_1(0-) = I_0 \quad \& \quad V_C(0-) = V_0$$

At $t(0+)$, $i_1(t) \& R$ gets connected to the $R_1 - L - C$ II ckt.


Find $V(s)$ & $v(t)$ across $R_1 - L - C$ II ckt.

Soln :- Transform N/W can be drawn as :-

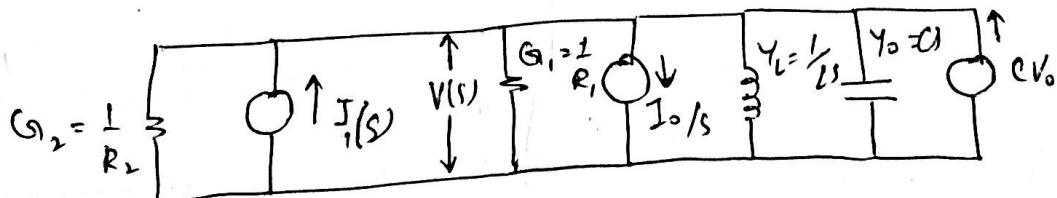

Total Xform current in the N/W is -

$$I(s) = I_1(s) - \frac{I_0}{s} + CV_0$$

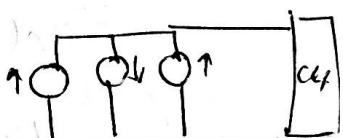

Total Xform admittance is given by -


$$Y(s) = G_1 + G_2 + \frac{1}{Ls} + Cs$$

$$V(s) = \frac{I(s)}{Y(s)} = \frac{I_1(s) - \frac{I_0}{s} + CV_0}{G_1 + G_2 + \frac{1}{Ls} + Cs}$$

$$\mathcal{L}^{-1}\{V(s)\} \rightarrow v(t)$$

$$G_1 + G_2 + \frac{1}{Ls} + Cs$$

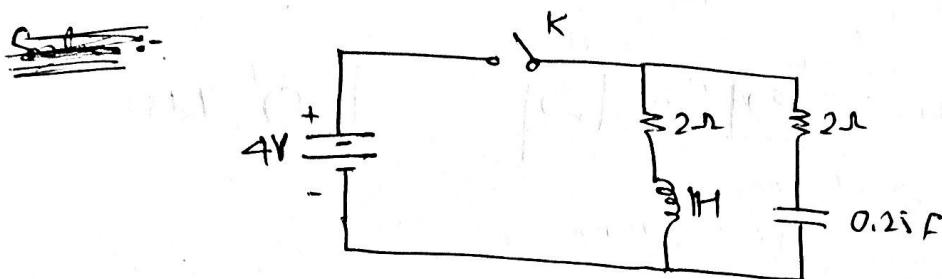(**) In given N/W, K is opened at (4)
 $t=0$. Draw transform N/W & find current
 $i(t)$ in the loop.




Soln Under S.S.

$$i_L(0-) = 2A$$

$$\& U_C(0-) = 4V \text{ d.c.}$$

\therefore Transform N/W is

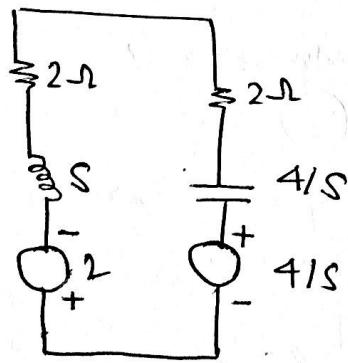


$$I(s) = \frac{V(s)}{Z(s)} = \frac{2 + 4/s}{2 + 2 + s + 4/s} = \frac{2(1+s)}{(s+2)^2} = \frac{2}{s+2}$$

in $i(t) = 2e^{-2t} \cdot u(t)$

Reciprocity Theorem :-

Given 2 N/W's (a) & (b), we have if

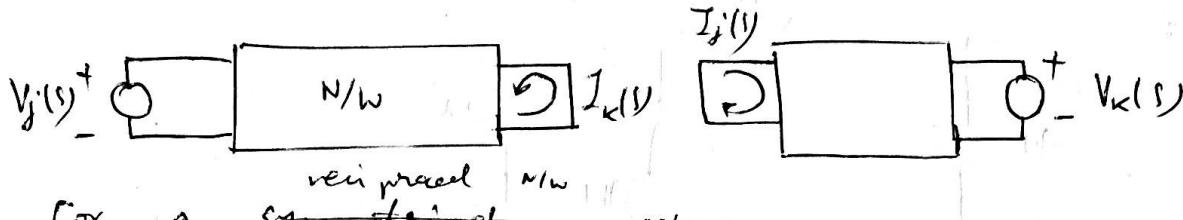

for a symmetrical N/W,

$$\frac{V_j(s)}{I_{k(s)}} = \frac{V_k(s)}{I_j(s)}$$

thus, $Z(s)$ matrix i.e., impedance matrix is symmetric.

Further if $V_j(s) = V_k(s)$, then $I_k(s) = I_j(s)$.

→ thus for a reciprocal N/W, we infer that
the ratio of response X-form to the excitation
X-form remains the same when we interchange
the positions of network & excitation in the
N/W.

→ this is principle of reciprocity.

→ Two N/W's are known as reciprocal N/W's.

- A N/W is reciprocal if :-
- i) The N/W is initially relaxed.
- ii) only linear elements are present in the N/W.
- iii) dependent or controlled source even if linear must be absent.